



K.S. SCHOOL OF ENGINEERING AND MANAGEMENT, BANGALORE - 560109
DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING
I SESSIONAL TEST QUESTION PAPER 2018 – 19 ODD SEMESTER
SET-B

USN									
-----	--	--	--	--	--	--	--	--	--

Degree : B.E
Branch : ECE
Course Title : Power Electronics
Duration : 90 Minutes

Semester : VII 'A' & 'B'
Date : 4-9-2019
Course Code : 15EC73
Max Marks : 30

Note: Answer ONE full question from each part

Q. No.	Question	Marks	K Level	CO mapping
PART-A				
1 (a)	Define power electronics. Identify its industrial applications.	5	K2 Understand	CO1
(b)	Identify the merits and demerits of power electronics as compared to conventional methods of power processing.	5	K2 Understand	CO1
(c)	Explain class B commutation.	5	K2 Understand	CO2
OR				
2 (a)	Explain Two Transistor Analogy of SCR. Using Two Transistor analogy derive an expression for anode current in terms of gate current.	5	K2 Understand	CO1
(b)	Explain the static characteristics of SCR.	5	K2 Understand	CO1
(c)	Discuss the different methods to turn ON Thyristor.	5	K2 Understand	CO2
PART-B				
3 (a)	With neat diagram, discuss the control characteristics of various power semiconductor devices.	5	K2 Understand	CO1
(b)	Discuss the Gate Characteristics of SCR with neat diagram.	5	K2 Understand	CO1
(c)	Explain Dynamic Turn OFF characteristics of SCR.	5	K2 Understand	CO2
OR				
4 (a)	Explain the peripheral effects caused by power electronics converters.	5	K2 Understand	CO1
(b)	Identify the components of total average power loss occurring in practical semiconductor switches? Discuss the need to compute these losses?	5	K2 Understand	CO1
(c)	A thyristor with latching current of 100mA is connected in series with a resistance of 10 ohms and inductance of 1 H. DC source voltage is 207 volt. Compute the minimum gate pulse width to turn on thyristor.	5	K2 Understand	CO2

Course In charge

Head Dept

Principal

57-91-19



K.S. SCHOOL OF ENGINEERING AND MANAGEMENT, BANGALORE - 560109
DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING
II SESSIONAL TEST QUESTION PAPER 2019 – 20 ODD SEMESTER
SET-A

USN									
-----	--	--	--	--	--	--	--	--	--

Degree : B.E
 Branch : ECE
 Course Title : Power Electronics
 Duration : 90 Minutes

Semester : VII 'A' & 'B'
 Date : 15-10-2019
 Course Code : 15EC73
 Max Marks : 30

Note: Answer ONE full question from each part

Q. No.	Question	Marks	K Level	CO mapping
PART-A				
1(a)	Draw the circuit diagram of RC Triggering circuit and illustrate its working with relevant waveforms.	5	Applying (K3)	CO2
(b)	With a neat circuit diagram and waveform, explain the working of single phase dual converter.	5	Understanding (K2)	CO3
(c)	Explain the working of single phase half wave controller with R load. Also derive the expression for RMS output voltage.	5	Applying (K3)	CO3
OR				
2(a)	Draw the circuit diagram of UJT Triggering circuit and illustrate its working with relevant waveforms.	5	Applying (K3)	CO2
(b)	Explain the working of semi converter (Half Bridge) with RL Load along with relevant circuit diagrams and waveforms.	5	Understanding (K2)	CO3
(c)	Explain the working of ON-OFF type AC voltage controller. Derive the expression for RMS output voltage.	5	Applying (K3)	CO3
PART-B				
3(a)	A UJT is used to trigger the thyristor whose minimum gate triggering voltage is 6.2 V. The UJT ratings are $\eta = 0.66$, $I_P = 0.5$ mA, $I_V = 3$ mA, $R_{B1} + R_{B2} = 5$ K Ω , leakage current = 3.2 mA, $V_P = 14$ V, $V_V = 1$ V. Oscillator frequency is 2 KHz and the capacitor $C = 0.04$ μ F. Design the circuit.	5	Applying (K3)	CO2
(b)	Explain the operation of single phase bidirectional AC voltage controller for resistive load with the help of neat circuit diagram and derive expression for rms output voltage.	5	Applying (K3)	CO3
(c)	An AC voltage controller has a resistive load of $R = 10\Omega$ and rms input voltage is 120 V, 50 Hz. The thyristor switch is ON for $n = 25$ cycles and OFF for $M = 75$ cycles. Calculate: rms output voltage, input power factor, average and rms thyristor current.	5	Applying (K3)	CO3
OR				

4(a)	Explain the working of half wave converter with RL load. Also derive the expression for average output voltage.	5	Applying (K3)	CO2
(b)	A single phase half wave ac voltage controller has an input voltage of 120 V and a load resistance of 5Ω . The firing angle of thyristor is 60° . Calculate average output voltage, rms output voltage, power factor.	5	Applying (K3)	CO3
(c)	With the help of circuit diagram, explain the operation of a single phase full converter with RL load. Derive expression for rms and average output voltages.	5	Applying (K3)	CO3

3

V. Mohan
Course In charge

[Signature]
Head - Dept

[Signature]
Principal



K.S. SCHOOL OF ENGINEERING AND MANAGEMENT, BANGALORE - 560109
DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING
III SESSIONAL TEST QUESTION PAPER 2019 – 20 ODD SEMESTER
SET-A

USN									
-----	--	--	--	--	--	--	--	--	--

Degree : B.E
Branch : ECE
Course Title : Power Electronics
Duration : 90 Minutes

Semester : VII 'A' & 'B'
Date : 25-11-2019
Course Code : 15EC73
Max Marks : 30

Note: Answer ONE full question from each part

Q. No.	Question	Marks	K Level	CO mapping
PART-A				
1(a)	Explain the operation of step-down chopper with R load. Also derive the expression for average and rms output voltage.	5	Applying (K3)	CO4
(b)	With a neat sketch and waveforms, explain the working of buck regulator.	5	Understanding (K2)	CO4
(c)	Illustrate the working of half bridge inverter with R load.	5	Applying (K3)	CO5
OR				
2(a)	For the step down chopper with source voltage of 230 V, load resistance of 10 Ω with a voltage drop across chopper of 2 V. Duty cycle is 0.4. Calculate i) average and rms output voltage ii) Chopper efficiency.	5	Applying (K3)	CO4
(b)	Explain the performance parameters of Inverters.	5	Understanding (K2)	CO4
(c)	Illustrate the working of full bridge inverter with RL load.	5	Applying (K3)	CO5
PART-B				
3(a)	Illustrate the working principle of step up chopper.	5	Applying (K3)	CO4
(b)	A step up DC chopper has an input voltage of 200 V and an output voltage of 250 V. The blocking period in each cycle of operation is 0.6 μsec. Calculate the period of conduction in each cycle.	5	Applying (K3)	CO4
(c)	The single phase half bridge inverter has the DC input of 48 V. The load resistance is 4.8 Ω. Determine the i) rms value of output voltage ii) RMS value of fundamental component iii) Total harmonic distortion	5	Applying (K3)	CO5
OR				
4(a)	Illustrate the working of class E chopper.	5	Applying (K3)	CO4
(b)	Illustrate the working of boost regulator.	5	Applying (K3)	CO4
(c)	With a neat sketch, illustrate the working of single phase thyristorized current source inverter.	5	Applying (K3)	CO5

5

 Course In charge

Head - Dept
 20/11/19

Principal