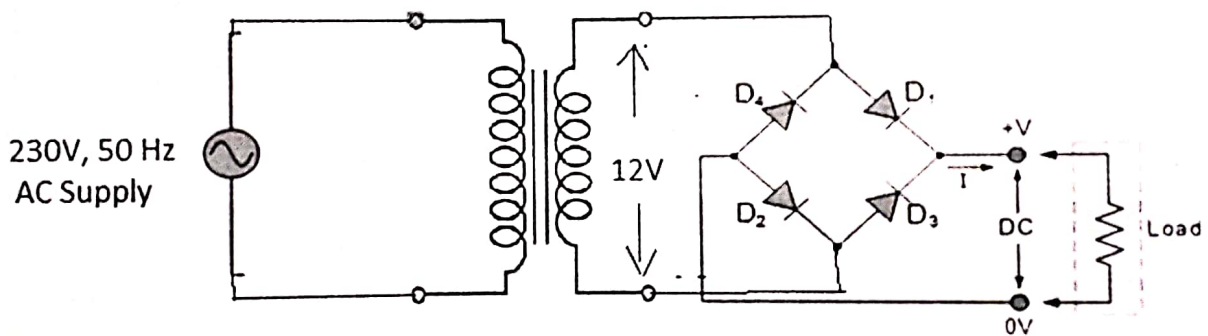


MINI PROJECT
TRANSFORMER APPLICATION

A Step down Transformer is a type of transformer, which converts a high voltage at the primary side to a low voltage at the secondary side. If we speak in terms of the coil windings, the primary winding of a Step down Transformer has more turns than the secondary winding i.e. $N_2 < N_1$

The step-down transformer reduces the AC voltage from high to low whereas the step-up transformer increases the AC voltage from low to high. In fullwave rectifier, we generally use a step-down transformer because the voltage needed for the diode is very small.

CIRCUIT DIAGRAM:



Here input voltage is 230V, 50Hz AC supply and step down transformer of 230/12V rating is used . Input to full wave bridge the rectifier circuit is 12V AC. Rectifier circuit converts AC to DC . Output of the rectifier circuit is connected to the load.

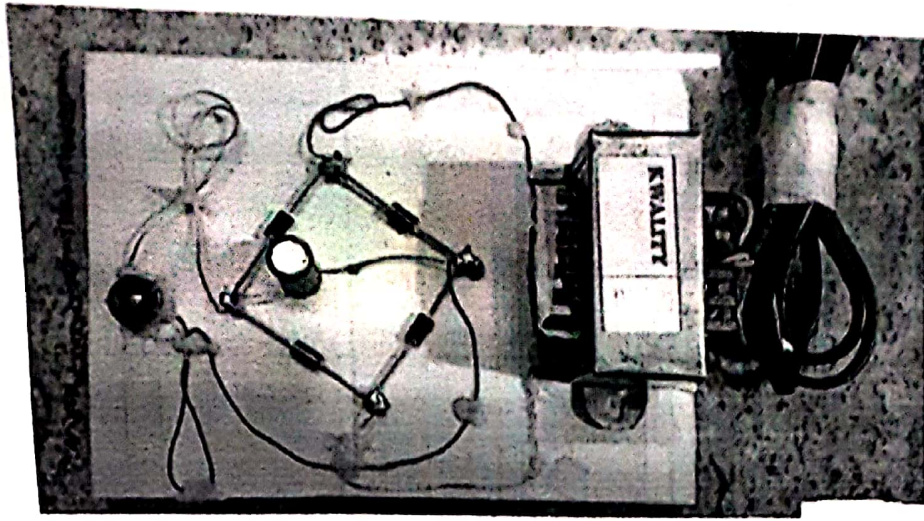


Fig: Miniproject Setup

Presented by:

Name	USN
1. Sanjay P Swamy	1KG19EE006
2. Dhanush Srinivas	1KG19EE002
3. Prathik P Shirali	1KG19EE005
4. S Praveen Kumar	1KG19EE009
5. Kovuri Dilli Babu	1KG18EE008

Prathik
Course In charge

[Signature]
Head of the Department
Associate Professor
Head of the Department
Department of Electrical & Electronics Engineering
and Management